



SCHOOL OF ELECTRONICS ENGINEERING

CAT - I (25/08/2024)

Fall Semester 2024 - 2025

B.Tech - in VLSI Design

Class Number: VL2024250104065

Course Name: BEVD204L, Electronic Circuits

Faculty-In-Charge: Abdul Majeed K K



Time : 09.30 AM - 11.00 AM

Max. Marks : 50

Slot : A1 + TA1

Answer ALL Questions

Assume data wherever necessary.

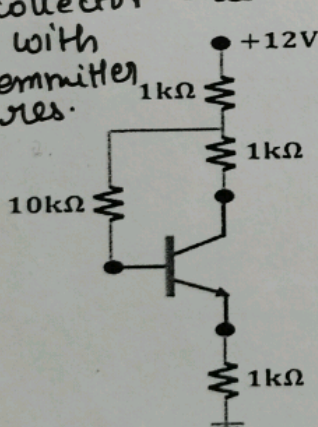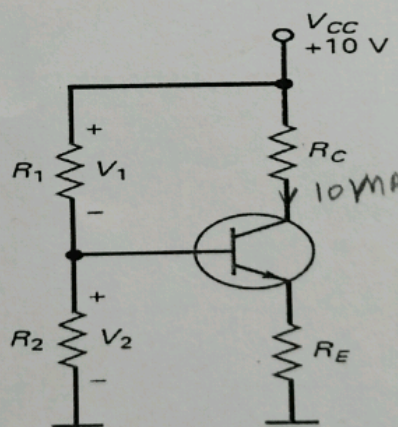Section - A		
S.No.	Question	Max. Marks
1.	<p>a). Define stability factor and derive the stability factor of <u>Common base BJT</u> configuration.</p> <p>b) What is mean by Operating point? Derive the <u>expression for the <math>I_B</math>, <math>I_C</math> and <math>V_{CE}</math> of the base biased with collector feedback BJT</u> circuits.</p>	10
2.	<p>a) A transistor having <math>\alpha = 0.99</math> and <math>V_{BE} = 0.7</math> is used in the circuit shown in Fig. 1 below. Calculate the currents <math>I_C</math>, <math>I_B</math>, <math>I_E</math> (4 M)</p> <p>collector bias with emitter res.</p>  <p>Fig. 1</p>  <p>Fig.2</p> <p>b) Determine the resistor values to meet this specification given below for the circuit shown in Fig.2 (6 M)</p> <p><math>V_{CC} = 10\text{ V}</math>, <math>I_C = 10\text{ mA}</math>, <math>V_{CE}</math> @ midpoint and <math>\beta = 100</math></p>	10
	<p>Calculate the base, collector, emitter currents, power dissipation and the C-E voltage for a common emitter circuit shown in Fig. 3. Assume <math>V_{BB} = 7\text{ V}</math>, <math>V_{CC} = 12\text{ V}</math>, <math>R_C = 4\text{ k}\Omega</math>, <math>R_B = 200\text{ k}\Omega</math> and <math>\beta = 300</math>. Calculate operating point using graphical method and find out <math>I_{CQ}</math> and <math>V_{CEQ}</math>.</p>	10

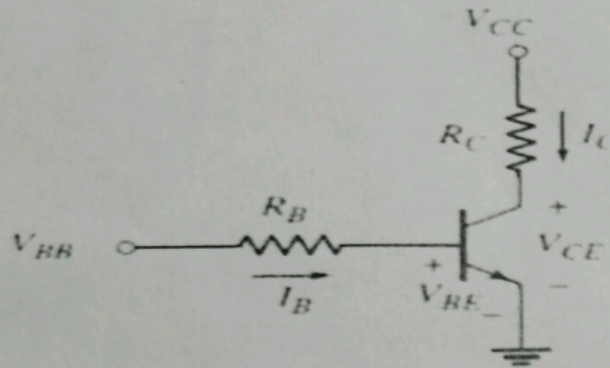


Fig.3

4. Consider a single stage CE amplifier with  $R_s = 1\text{ k}\Omega$ ,  $R_1 = 50\text{ K}\Omega$ ,  $R_2 = 2\text{ K}\Omega$ ,  $R_c = 1\text{ K}\Omega$ ,  $R_L = 1.2\text{ K}\Omega$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1\text{ K}$ ,  $h_{oe} = 25\mu\text{ A/V}$  and  $h_{re} = 2.5 \times 10^{-4}$ , as shown in Fig.4. Find  $A_i$ ,  $R_i$ ,  $A_v$ ,  $A_{vs}$ ,  $A_{Is}$  and  $R_o$ .

10

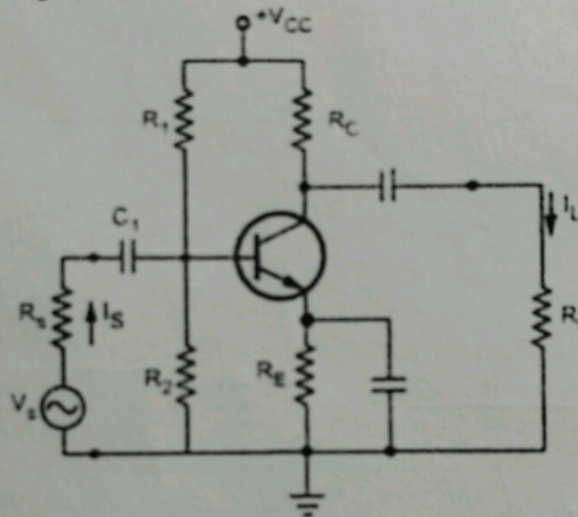


Fig.4

5. Design and implement a circuit to realise the following wave form given in Fig. 5 using OP-AMP

10

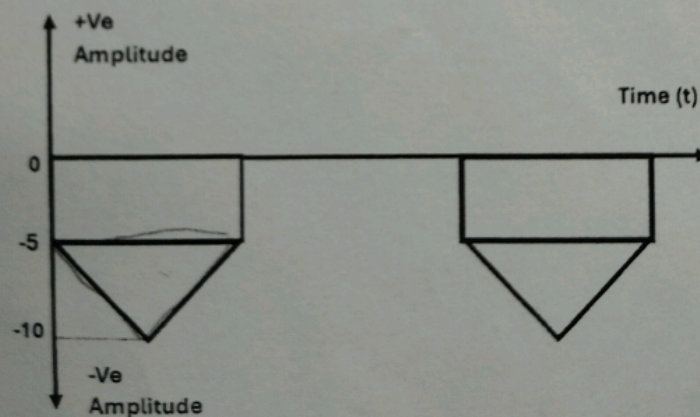


Fig.5